



# Lab 7 pipeline

---


楊豐賓

# Design a simple operation

- **Out = max(in\_1, in\_2) \* max(in\_3, in\_4)**
  - in\_1, in\_2, in\_3, in\_4: 48 bits unsigned number
  - Out: 96 bits unsigned number
- Large bit-width multiplier is costly

# Naïve design

- No pipeline => long critical path

 


critical path = 48-bits comparator & mux + 48-bits multiplier = 7ns  
> cycle time you will fail !!

# Simple pipeline design

- Simply separate adder and multiplier

assume cycle time: 5ns

 

critical path = max(48-bits comparator & mux, 48-bits multiplier) = 6ns > cycle time

- Beats naïve design, but still faces negative slack

- Let's go back to elementary school

- ```
out = P1 + P2 * 10 + P3 * 10 + P4 * 100
```

NYCU.EE, Hsinchu, Taiwan

# For our binary case

- Example: Partition operands A and B into two parts

$$- A[47:0] * B[47:0]$$

$$= (A[47:24] * 2^{24} + A[23:0]) * (B[47:24] * 2^{24} + B[23:0])$$

$$= A[47:24] * B[47:24] * 2^{48}$$

$$+ A[47:24] * B[23:0] * 2^{24}$$

$$+ B[47:24] * A[23:0] * 2^{24}$$

$$+ A[23:0] * B[23:0]$$

P1 =



P2 +

P3 +

P4 +

out

  
$$\begin{array}{r} A[47:24] \quad A[23:0] \\ * \quad B[47:24] \quad B[23:0] \\ \hline \end{array}$$


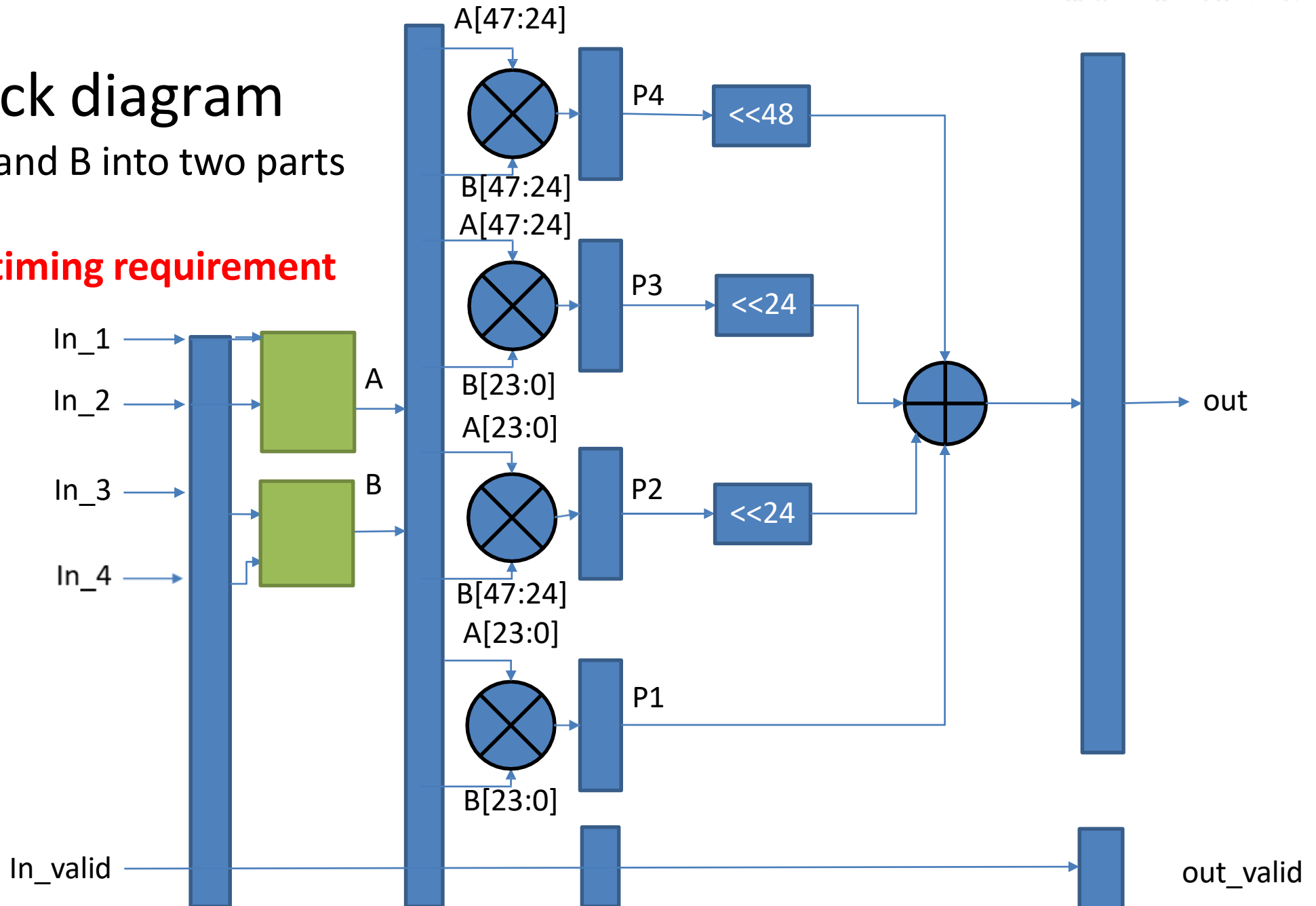
# Example block diagram

For partitioning A and B into two parts

✗ You won't pass timing requirement using this design




# But...

- The critical path of the example block diagram is 24-bit multiplier
  - What if that's still not enough ?
    - Further partition the combinational circuit on the critical path
  - What you have to do in this lab
    - Refer to the example block diagram in the last page
    - Design a pipeline that partitions the multiplication of operands A and B into **three parts**
- ✘ You won't pass timing requirement if you only follow example block diagram



# Fill in the blank !

 

# P\_MUL.sv

| Input Signal | Bit Width | Definition                                                                     |
|--------------|-----------|--------------------------------------------------------------------------------|
| clk          | 1         | clock                                                                          |
| rst_n        | 1         | Asynchronous active-low reset                                                  |
| in_1         | 48        | unsigned inputs                                                                |
| in_2         | 48        | unsigned inputs                                                                |
| in_3         | 48        | unsigned inputs                                                                |
| in_4         | 48        | unsigned inputs                                                                |
| in_valid     | 1         | in_valid = 1 indicates one valid input will be high for 1000 continuous cycles |

**in\_1, in\_2 in\_3 and  
in\_4 will be given  
in one cycle**

| Output Signal | Bit Width | Definition                                                              |
|---------------|-----------|-------------------------------------------------------------------------|
| out_valid     | 1         | out_valid = 1 indicates one valid output<br><b>can be discontinuous</b> |
| out           | 96        | unsigned output                                                         |

# Specs


- Input and output signals are **unsigned**
- All output ports have to be reset to **0**
- 01\_RTL **PASS**
- 02\_SYN clock period = **4.5ns**, timing slack must be **MET**, no **error** and **latch**
- 03\_GATE **PASS**, no **error** and **timing violation**

# Something you should know

- The critical path of large bit-width multiplier is long, you must use pipeline
- Input and output numbers are extremely big, so debugging by nWave is hard
- **Longer critical path will induce longer synthesis time**
- It's simpler to refer to the provided block diagram, but you can try to design your own pipeline. Just **Think twice before writing your code !**

# Output & Waveform

- Waveform

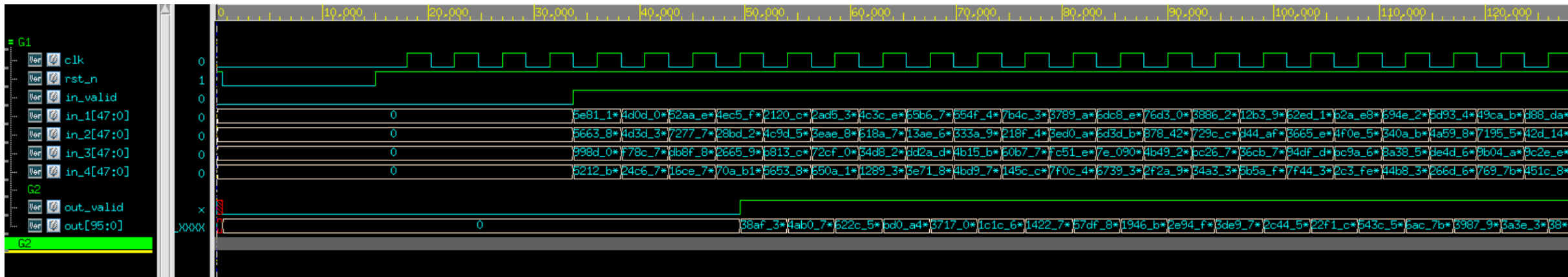

in\_valid will be high for 1000 continuous cycles  
 out\_valid should be high for 1000 cycles, but it can be discontinuous

# Command

- `tar -xvf ~dcsTA01/Lab07.tar`
- Upload
  - `cd 09_upload`
  - `./01_upload`
  - `./02_download demoX`

DEMO1: 4/25 17:30:00

DEMO2: 4/26 23:59:59