

# DCS Lab4

---

## Sequential Circuit

# Sequential Circuit

- Different from combinational circuit, sequential circuit will synthesize **registers** which can store previous data.

```
always @(posedge clk or negedge rst_n) begin
    if(!rst_n)
        a <= 0;
    else
        a <= a + 1;
end
```

← Sequential circuit

```
assign a = a + 1;

always @(*) begin
    a = a + 1;
end

always @(*) begin
    if(a > b) a = b;
    else a = a;
end
```


← Combinational circuit

# Waveform Difference

- Combinational Circuit

```
always@(*)begin
    if(in_valid) out_data = in_data;
    else out_data = 0;
end

 
assign out_data = (in_valid) ? in_data : 0;
```


 
# Waveform Difference


- Sequential Circuit

```
always@(posedge clk or negedge rst_n)begin
    if(!rst_n)
        out_data <= 0;
    else begin
        if(in_valid) out_data <= in_data;
        else out_data <= 0;
    end
end
end
```


 
# Image Subtract

- Residual Image
- Show objects in the image (image – background)



# Image Subtract

img1

15	10	11
12	12	14
13	13	13

img2

9	5	1
6	4	3
5	9	1

-

=


6	5	10
6	8	11
8	4	12

# Seq.sv

Input Signal	Bit Width	Definition
clk	1	Clock
rst_n	1	Asynchronous active-low reset
in_valid	1	High when input is valid
in_image	4	Pixel values of two images (Raster Scan Order)

Output Signal	Bit Width	Definition
out_valid	1	High when output is valid
out_diff	4	Pixel values of difference => <b>img1 – img2</b> (Raster Scan Order)

# Raster Scan Order

 




# Spec of 01\_RTL

- **for\_loop** is forbidden
- All output should be reset after the reset signal is asserted
- The **out\_valid** should not be raised when **in\_valid** is high.
- When out\_valid is low, all output should be reset to 0
- The out\_valid should be high within **100 cycles** after in\_valid pull low
- Cannot name your registers or wires with those words, such as **\*error\***, **\*congratulation\***, **\*latch\*** or **\*fail\***, which will cause demo fail


# Spec of 02\_SYN & 03\_GATE

- The synthesis result (syn.log) cannot include **any error and latch**
- The slack in the end of timing report should be **non-negative** and **MET**
- 03\_GATE simulation need **pass** and without **timing violation** warning


# Waveform

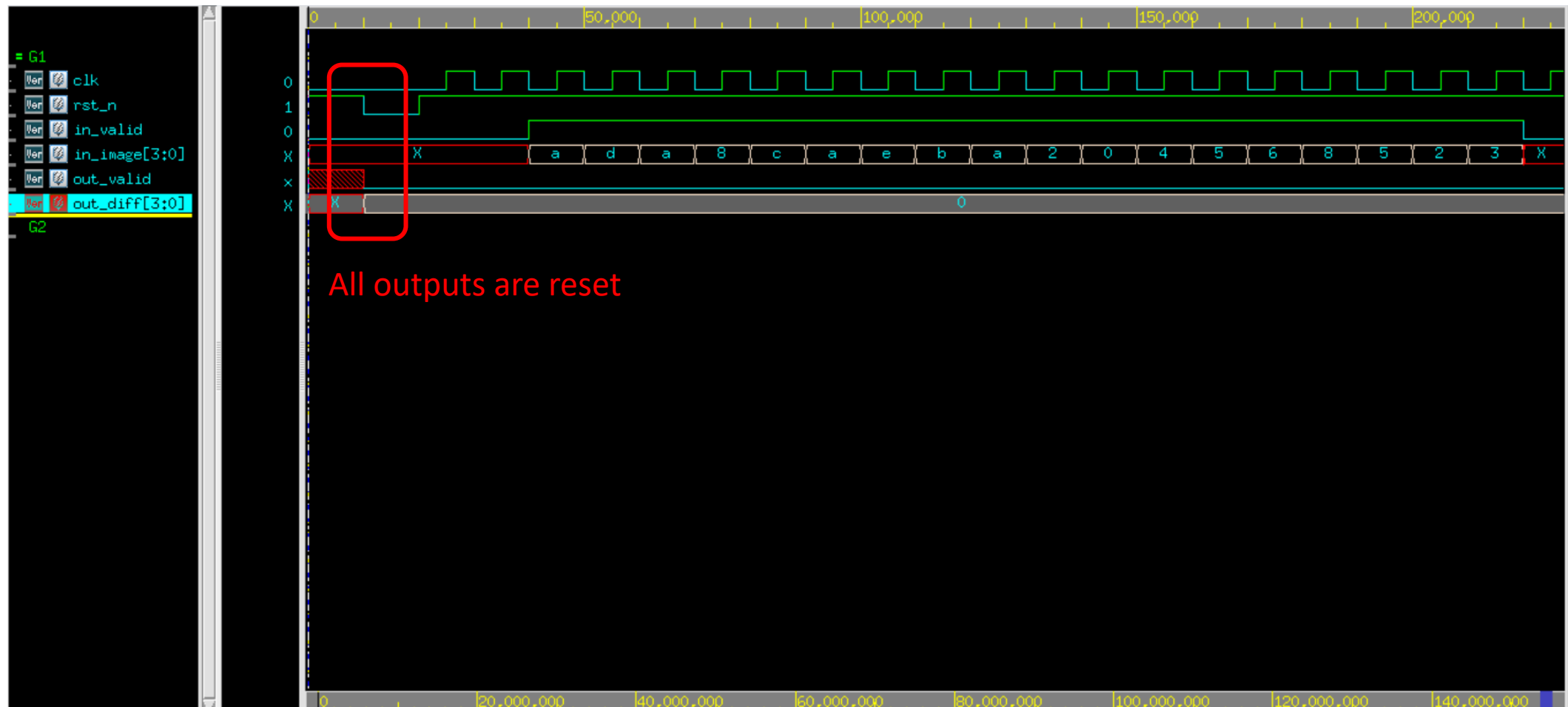

# Waveform

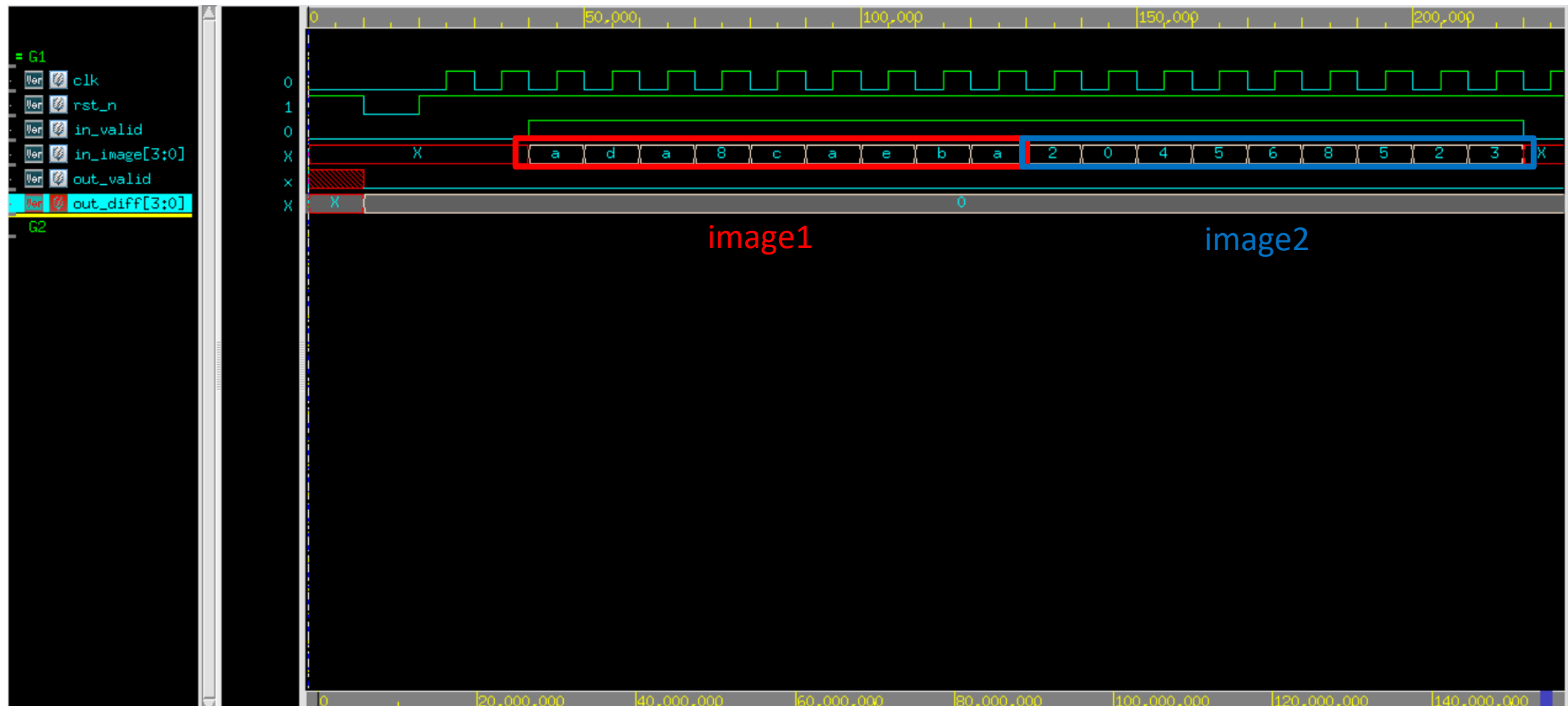

# Waveform

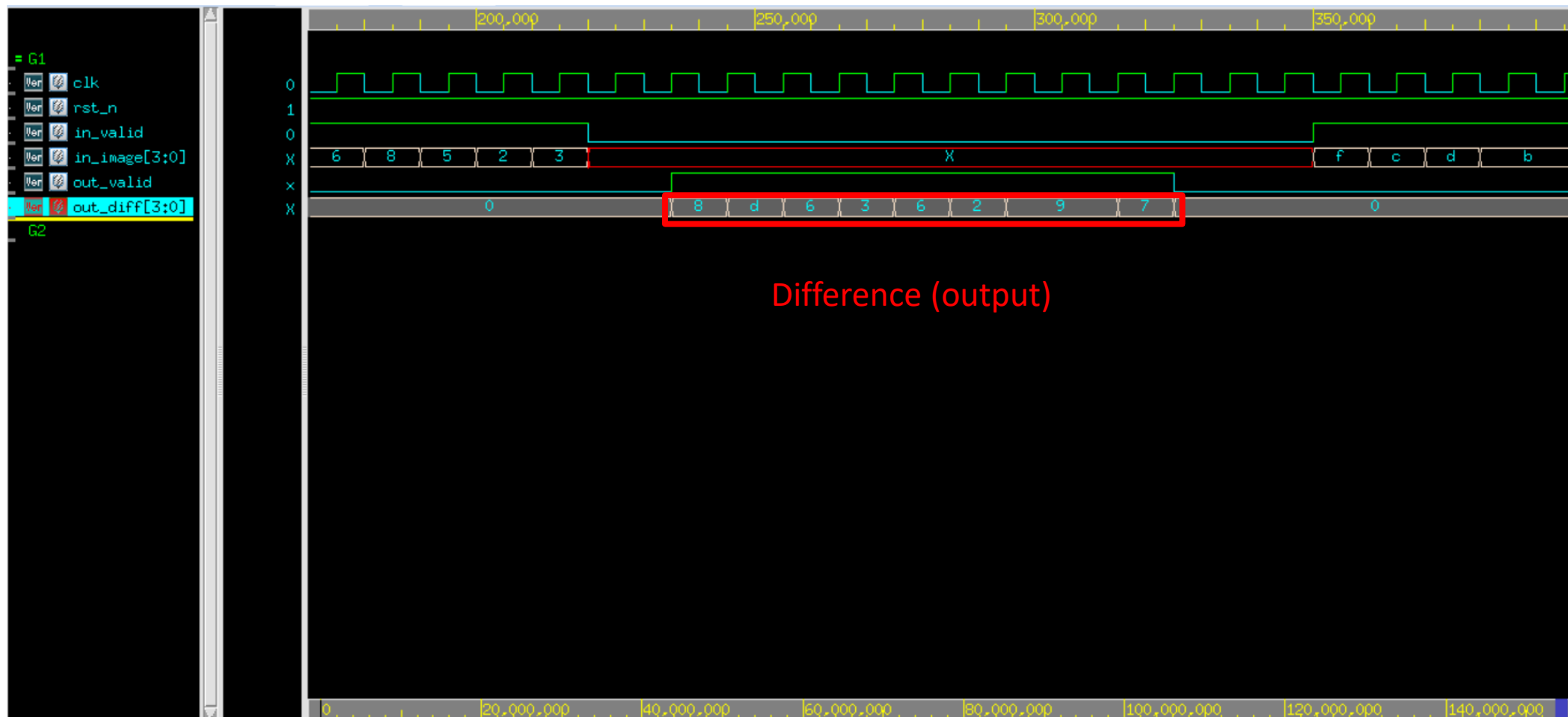

# Command

- `tar -xvf ~dcsta01/Lab04.tar`
- 02\_SYN need
  - No Latch
  - No error
  - No timing violation (MET)
- 03\_GATE
  - Simulation need **pass** and **no timing violation**

**DEMO1: 3/21 17:30:00**

**DEMO2: 3/22 23:59:59**